

Name: _____

Grade: _____

/10

- [5] 1) Design 2-b binary multiplier using one decoder and NAND gates. The bits of the input numbers and the output product are as given in the following equation:

$$A1 A0 \times B1 B0 = P3 P2 P1 P0$$

- [1] 1.a) Fill the following truth table that defines the relationship between the two 2-b numbers (total of 4 binary inputs) and the 4-b product.
- [1] 1.b) Find the minterm expansion for each of the output bits directly from the truth table.

Inputs Numbers		Output Product	
A1A0	B1B0	P3 P2 P1 P0	decimal


P3 = _____

P2 = _____

P1 = _____

P0 = _____

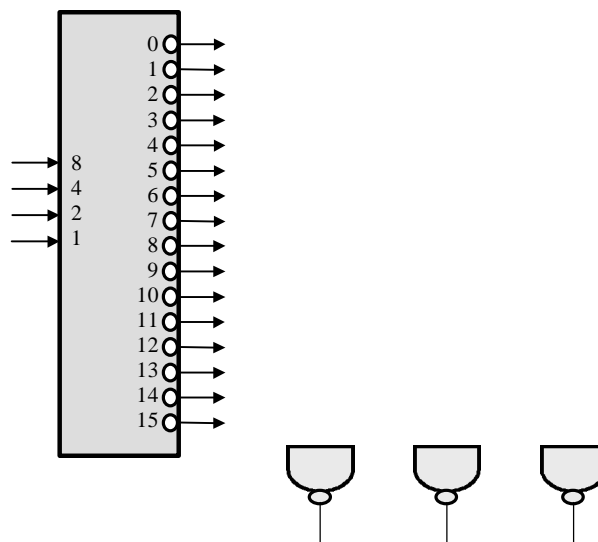- [3] 1.c) Realize the above outputs using the following 4-16 decoder and NAND gates.



Name:

Grade:

/10

- [5] 2) Show the necessary input connections to realize the following Boolean expression using the 8-to-1 multiplexer shown below. Show all input and output connections.

$$F(A,B,C,D) = \sum m(1,3,4,5,8,10,12)$$

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

