

Name: _____


Grade: _____

/10

[10] 1) The following state table describes the behavior of a Moore sequential machine with 4 states A/B/C/D, 1 input X and 2 outputs Z1Z2.

[2] 1.a) From the next state table, complete the state graph

Present State	Next State		Outputs Z1Z2
	X= 0	X= 1	
A	B	B	10
B	C	D	01
C	A	C	11
D	D	A	00

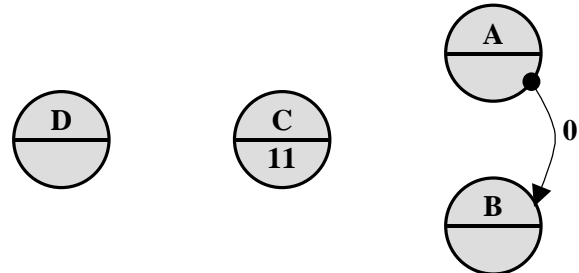



[+1] 1.b) Describe the behavior of the above Moore machine in English. That is what sequences the outputs will go through if the input changes to a certain value in a certain state?

[2] 1.c) Use the indicated binary assignments to complete the transition table below.

[2] 1.d) Fill the next state maps for each of the two required flip-flops.

[2] 1.e) It is required to use a TFF to implement Q1 and a JKFF to implement Q2. Fill the T and JK input excitation maps from the next state maps.

Present State	Next State		Outputs Z1Z2
	X= 0	X= 1	
00			
01			
11			
10			

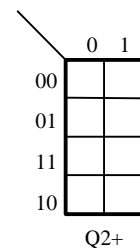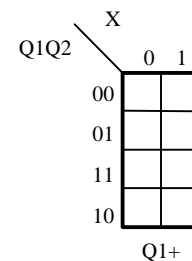

[2] 1.f) Write the minimized input expressions for each of the two flip-flops.

